

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L1	$I_{k1''} = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
1Q8	LTN-10B $I_n = 10 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 45 \text{ A}$	
	$Z_s(0,4s) = 4.62 \text{ Ohm}$, $I_a = 50 \text{ A}$, $R(50V/5s) = 1.00 \text{ Ohm}$		
1L9	1-CXKE-R 3x1,5 $I_z = 20 \text{ A}$ $t_m = 113^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 652 \text{ A}$ $I_{p1} = 941 \text{ A}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($926 \text{ mOhm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$)
2201	Vývod $I = 10 \text{ A} \times 8 = 10 \text{ A}$ $I = 10.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 652 \text{ A}$ $I_{p1} = 941 \text{ A}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($926 \text{ mOhm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$)

Zapojení	Přístroj	Poznámka
1B1	Síť TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$
	TN-C TN-S	
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
	3f L2	$I_{k1''} = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$
2Q8	LTN-10B $I_n = 10 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 45 \text{ A}$
2L9	$Z_s(0,4s) = 4.62 \text{ Ohm}$, $I_a = 50 \text{ A}$, $R(50V/5s) = 1.00 \text{ Ohm}$ 1-CXKE-R 3x1.5 $I_z = 20 \text{ A}$ $t_m = 113^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 652 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($926 \text{ mOhm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$) $i_{p1} = 941 \text{ A}$
2202	Vývod $I = 10 \text{ A}$ xB = 10 A $I = 10.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 652 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($926 \text{ mOhm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$) $i_{p1} = 941 \text{ A}$

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L3	$I_{k1''} = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
3Q8	LTN-10B $I_n = 10 \text{ A}$ $Z_s(0,4s) = 4.62 \text{ Ohm}$, $I_a = 50 \text{ A}$, $R(50V/5s) = 1.00 \text{ Ohm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 45 \text{ A}$	
3L9	1-CXKE-R 3x1.5 $I_z = 20 \text{ A}$ $t_m = 113^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 473 \text{ A}$ $I_{p1} = 683 \text{ A}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($1.19 \text{ Ohm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$)
2203	Vývod $I = 10 \text{ A} \times B = 10 \text{ A}$ $I = 10.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.4\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 473 \text{ A}$ $I_{p1} = 683 \text{ A}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($1.19 \text{ Ohm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$)
	L3		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L1	$I_{k1}'' = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
4Q8	LTN-10B $I_n = 10 \text{ A}$ $Z_s(0,4s) = 4.62 \text{ Ohm}$, $I_a = 50 \text{ A}$, $R(50V/5s) = 1.00 \text{ Ohm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 45 \text{ A}$	
4L9	1-CXKE-R 3x1,5 $I_z = 20 \text{ A}$ $t_m = 113^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_k'' = 473 \text{ A}$ $I_{p1} = 683 \text{ A}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($1.19 \text{ Ohm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$)
2204	Vývod $I = 10 \text{ A} \times B = 10 \text{ A}$ $I = 10.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.4\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1}'' = 473 \text{ A}$ $I_{p1} = 683 \text{ A}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($1.19 \text{ Ohm} < 4.62 \text{ Ohm}$, $2/3 Z_s = 3.08 \text{ Ohm}$)
	L1		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	<u>LTN-32B</u> $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	<u>1-CXKE-R 5x6</u> $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	<u>Sběrnice</u> $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L2	$I_k1'' = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
5F18	<u>DLI-16B-1N-030AC</u> $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5xI_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$		
5L9	<u>1-CXKE-R 3x2,5</u> $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2205	<u>Vývod</u> $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L2		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L3	$I_k1'' = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
6F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$		
6L9	1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2206	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L3		

Zapojení	Přístroj	Poznámka
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$
	TN-C TN-S	
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
	3f L1	$I_k1'' = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$
7F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$
7L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.33 \text{ kA}$
2207	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $\cos \phi_i = 0.95$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$I_k1'' = 921 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.33 \text{ kA}$
	L1	

Zapojení	Přístroj	Poznámka	
1B1	Síť TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L2	$I_k1'' = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
8F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$		
8L9	1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2208	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L2		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L3	$I_k1'' = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
9F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$		
9L9	1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2209	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L3		

Zapojení	Přístroj	Poznámka
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$
	TN-C TN-S	
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
	3f L1	$I_k1'' = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$
10F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$
10L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.33 \text{ kA}$
2210	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 921 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.33 \text{ kA}$
	L1	

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L2	$I_k1'' = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
11F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$		
11L9	1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2211	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L2		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L3	$I_k1'' = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
12F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$		
12L9	1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 20 m, (C) $dU = 2.3 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2212	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 235 \text{ V}$ ($U_n + 1.6\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 921 \text{ A}$ $I_{p1} = 1.33 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($717 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L3		

Zapojení	Přístroj	Poznámka
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$
	TN-C TN-S	
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
	3f L1	$I_k1'' = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$
13FI8	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$
13L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$
2213	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$
	L1	

Zapojení	Přístroj	Poznámka
1B1	Síť TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$
	TN-C TN-S	
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
	3f L2	$I_{k1''} = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$
14FI8	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$
14L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$
2214	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L3	$I_{k1''} = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
15FI8	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
15L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 694 \text{ A}$ $I_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2215	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 694 \text{ A}$ $I_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L3		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $i_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $i_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L1	$I_k1'' = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$	
16F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
16L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 694 \text{ A}$ $i_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2216	Vývod $I = 16 \text{ A} \times B = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 694 \text{ A}$ $i_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L1		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ $i_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ $i_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L2	$I_k1'' = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$	
17FI8	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
17L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 694 \text{ A}$ $i_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2217	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 694 \text{ A}$ $i_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L2		

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ $i_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ $i_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L3	$I_{k1''} = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$	
18F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
18L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 694 \text{ A}$ $i_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2218	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 694 \text{ A}$ $i_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L3		

Zapojení	Přístroj	Poznámka
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$
	TN-C TN-S	
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
	3f L2	$I_{k1''} = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$
19FI8	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$
19L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$
2219	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$

Zapojení	Přístroj	Poznámka	
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_{k''} = 2.76 \text{ kA}$	
	TN-C TN-S		
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$	
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_{k''} = 2.59 \text{ kA}$ $I_p = 3.74 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$)
	3f L3	$I_{k1''} = 2.56 \text{ kA}$ $I_{p1} = 3.70 \text{ kA}$	
20F18	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$	
20L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_{k1''} = 694 \text{ A}$ $I_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
2220	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_{k1''} = 694 \text{ A}$ $I_{p1} = 1.00 \text{ kA}$	O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$)
	L3		

Zapojení	Přístroj	Poznámka
1B1	Sít TN $I_n = 100 \text{ A}$ $U_2 = 242/420 \text{ V}$ $dU = 1.0 \%$	$I_k'' = 2.76 \text{ kA}$
	TN-C TN-S	
1Q3	LTN-32B $I_n = 32 \text{ A}$ $Z_s(0,4s) = 1.43 \text{ Ohm}$, $I_a = 161 \text{ A}$, $R(50V/5s) = 310 \text{ mOhm}$	$I_{cn} = 10 \text{ kA}$ $I_i = 144 \text{ A}$
1L4	1-CXKE-R 5x6 $I_z = 44 \text{ A}$ $t_m = 105^\circ \text{ C}$ 2 m, (B) $dU = 0.1 \%$ $I^2 t < k^2 S^2$	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
1B6	Sběrnice $B = 0.25$ $U = 416 \text{ V}$ ($U_n + 3.9\%$)	$I_k'' = 2.59 \text{ kA}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($381 \text{ mOhm} < 1.43 \text{ Ohm}$, $2/3 Z_s = 953 \text{ mOhm}$) $i_p = 3.74 \text{ kA}$
	3f L1	$I_k1'' = 2.56 \text{ kA}$ $i_{p1} = 3.70 \text{ kA}$
21FI8	DLI-16B-1N-030AC $I_n = 16 \text{ A}$ $I_{dn} = 0.03 \text{ A}$	$I_{cn} = 10 \text{ kA}$ $I_i = 72 \text{ A}$
21L9	$Z_s(0,4s) = 1.54 \text{ kOhm}$, $5 \times I_{dn} = 0.15 \text{ A}$, $R(50V/5s) = 1.7 \text{ kOhm}$ 1-CXKE-R 3x2,5 $I_z = 28 \text{ A}$ $t_m = 110^\circ \text{ C}$ 30 m, (C) $dU = 3.4 \%$ $I^2 t < k^2 S^2$	$I_k1'' = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$
2221	Vývod $I = 16 \text{ A} \times 8 = 16 \text{ A}$ $I = 16.0 \text{ A}$ $U = 232 \text{ V}$ ($U_n + 0.5\%$) $B = 1$	$\cos \phi_i = 0.95$ $I_k1'' = 694 \text{ A}$ O.K. $Z_{sv} < Z_s(0,4s)$ ($883 \text{ mOhm} < 1.54 \text{ kOhm}$, $2/3 Z_s = 1.03 \text{ kOhm}$) $i_{p1} = 1.00 \text{ kA}$
	L1	